

Tutorial - 4

① JFET (Velocity)

Page No.: 1

Date:

youva

- ① A JFET has following parameters $I_{DSS} = 32 \text{ mA}$, $V_{GS(\text{off})} = -8 \text{ V}$, $V_{GS} = -4.5 \text{ V}$, $I_D = C1$


$$I_D = I_{DSS} \left[1 + \frac{V_{GS}}{V_{GS(\text{off})}} \right]^2$$

$$= 32 \left[1 - \frac{(-4.5)}{(-8)} \right]^2 \text{ mA}$$

$$= \underline{6.12 \text{ mA}}$$

② $I_{DSS} = 12 \text{ mA}$

$V_{GS(\text{off})} = -5 \text{ V}$

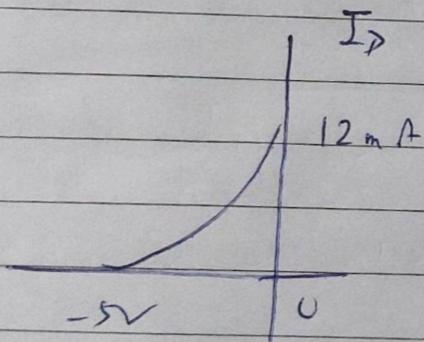

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_{GS(\text{off})}} \right]^2$$

$$= 12 \left[1 + \left(\frac{V_{GS}}{5} \right)^2 \right] \text{ mA}$$

Q A JFET has a drain current of 5 mA.
 $I_{DSS} = 10$, $V_{GS(\text{off})} = -6V$

$$V_{GS} = (?)$$

$$V_P = (?)$$


$$\rightarrow I_D = I_{DSS} \left[1 + \frac{V_{GS}}{V_{GS(\text{off})}} \right]^2$$

$$5 = 10 \left[1 + \frac{V_{GS}}{6} \right]^2$$

$$1 + \frac{V_{GS}}{6} = \sqrt{2} = 0.707$$

$$\rightarrow V_{GS} = 6 \times (-0.293) \\ = \underline{-1.76V}$$
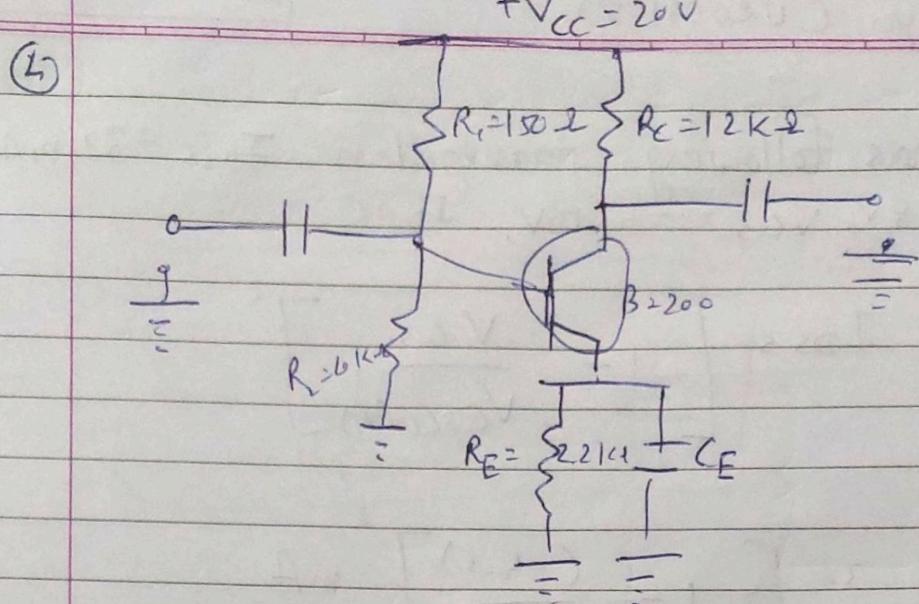
$$\rightarrow V_P = -V_{GS(\text{off})} \\ = -(-6) = \underline{6V}$$



Voltage gain with C_E , without C_L .

$$\rightarrow S_0, V_{R_2} = \frac{V_{CC}}{R_1 + R_2} \times R_2$$

$$= \frac{20}{170} \times 20$$

$$= \underline{2.35 \text{ V}}$$

$$\rightarrow S_0, V_B = V_2 - V_{BE}$$

$$= 2.35 - 0.7$$

$$= \underline{1.65 \text{ V}}$$

$$\rightarrow \text{Now Current in emitter } I_E = \frac{V_E}{R_E}$$

$$= \frac{1.65}{2.2 \text{ k}\Omega} = \underline{0.75 \text{ mA}}$$


of
Resistor at emitter

$$\rightarrow S_0 \gamma = \frac{25 \times 10^{-3} \text{ V}}{0.75 \times 10^{-3} \text{ A}} = \underline{33.3 \text{ }\Omega$$

(i) With CE \Rightarrow Voltage gain $A_v = \frac{R_C}{r_e} = \frac{12 \times 10^3 \Omega}{33.3 \Omega} = 360$

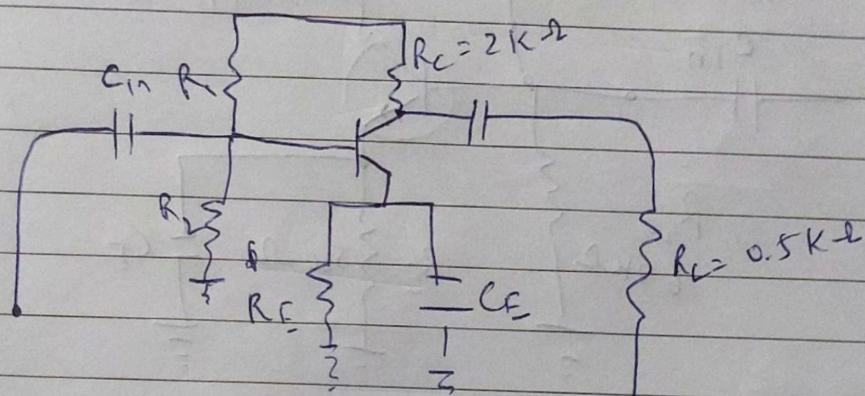(ii) Without CE \Rightarrow Voltage gain $A_v = \frac{R_C}{r_e + h_E} = \frac{12 \times 10^3}{2.2 \times 10^3 + 33.3} = 5.38$

⑤ Find Voltage gain, $\beta = 60$, $R_m = 1 \text{ k}\Omega$



$$R_{AC} = R_C \parallel R_L$$

$$\frac{1}{R_{AC}} = \frac{1}{R_C} + \frac{1}{R_L}$$


$$\frac{1}{R_{AC}} = \frac{1}{2} + \frac{1}{0.5}$$

$$R_{AC} = \frac{2 \times 0.5}{2 + 0.5}$$

$$= \underline{\underline{0.4 \text{ k}\Omega}}$$

$$\text{Voltage gain} = \beta \times \frac{R_{AC}}{R_m} = 60 \times \frac{0.4 \text{ k}\Omega}{1 \text{ k}\Omega} = 24.$$

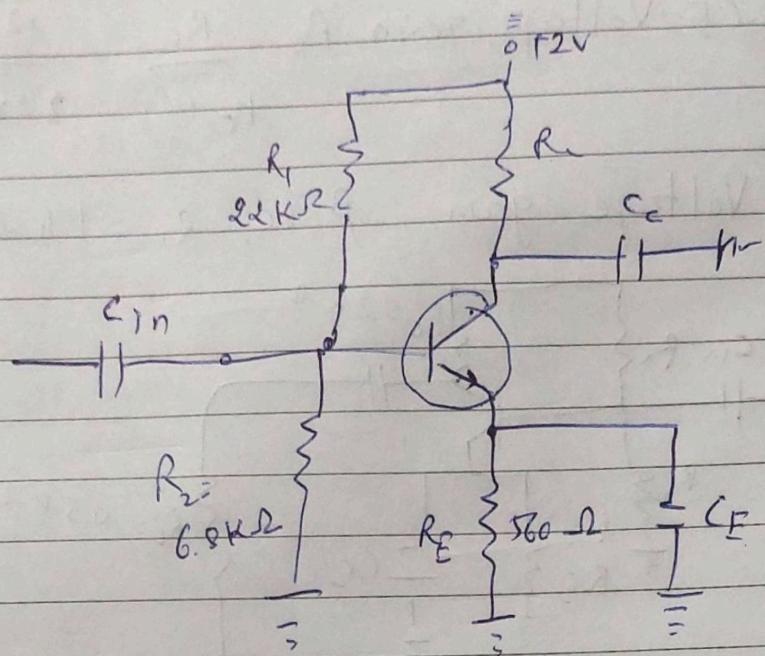(6) Select a suitable value for emitter bypass capacitor in Fig shown if freq over 2 kHz to 10 kHz



$$X_{C_E} = \frac{R_E}{10}$$

$$f_{m_n} = 2 \text{ kHz}, R_E = 560 \Omega$$

$$\therefore X_{C_E} = 56 \Omega$$

$$\therefore \frac{1}{2 \pi C_E} = 56$$

$$\therefore C_E = \frac{1}{2 \times \pi \times f_{m_n} \times 56}$$

$$= \frac{1}{2 \times 3.14 \times 2 \times 10^3 \times 56} = 1.63 \times 10^{-6} F$$

$$= 1.63 \mu F$$

(7)

$$V_{CC} = 20 \text{ V}$$

$$R_C = 2 \text{ k}\Omega$$

$$\beta = 50$$

$$V_{BE} > 0.2 \text{ V}$$

$$R_I = 100 \text{ k}\Omega$$

$$R_E = 100 \Omega$$


$$V_2 = \frac{V_{CC}}{R_1 + R_2}$$

$$I_E = \frac{V_2 - V_E}{R_E}$$

$$I_C \approx I_E$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

as R_2 is not given, so we can't find.

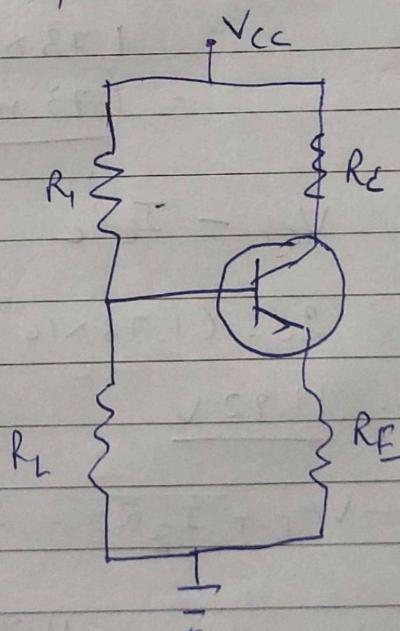

(8)

$$V_{CC} = 15V$$

$$V_{BB} = 0.7V$$


$$\beta = 100$$

$$V_{CB} \approx 0$$

$$V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) \times R_2$$

$$= \frac{15}{200} \times 100$$

$$= 7.5V$$

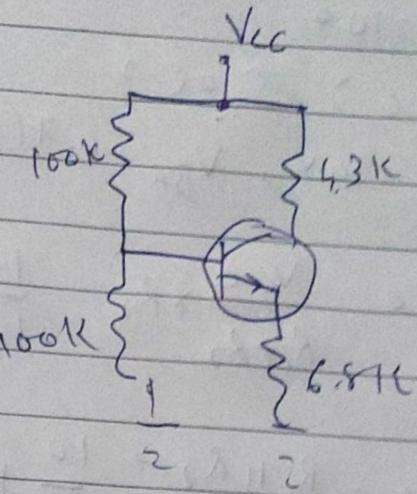

$$V_2 = V_{BE} + I_E R_E$$

$$I_B = \frac{7.5 - 0.7}{R_E}$$

$$\frac{6.8}{6.8 \times 10^3} = 1 \times 10^{-3}$$

$$= 1 \approx I_C$$

$$V_{CB} = V_{CC} - I_C (R_{CT} + R_E)$$

$$= 15 - 10^{-3} (11.1 \times 10^3)$$

$$= 15 - 11.1$$

$$= \underline{3.9V}$$

①

$$\beta = 100$$

$$V_{CE} \approx I_c \cdot R_E \\ V_{CC} = 10 \text{ V}, V_{BE} = 0.7 \text{ V (Silicon)}$$

$$E_B = \frac{V_{CC}}{R_1 + R_2} \times R_2 = \frac{10}{15} \times 5 \rightarrow \frac{10}{3}$$

$$R_o = R_1 || R_2 = \frac{10}{3} \text{ k}\Omega$$

$$I_B = \frac{E_B - V_{BE}}{\phi R_o + \beta X} = \frac{10/3 - 0.7}{\frac{10}{3} + 100 \times 0.5 \text{ k}\Omega}$$

$$\frac{2.6}{53.3 \text{ k}\Omega}$$

$$= \frac{2.6}{533} \times 10^{-3}$$

$$I_B = 0.048 \text{ mA}$$


$$I_C = 100 \times 0.048 = 4.8 \text{ mA}$$

$$V_{CB} = V_{CC} - I_C (R_E + R_E) \\ = 10 - 4.8 \times 10^{-3} (0.5 \times 10^3)$$

$$= 10 - 2.2$$

$$= \underline{2.8 \text{ V}}$$

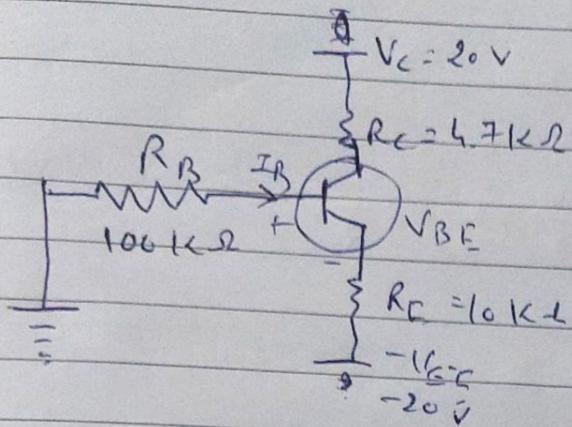(10) For the emitter biased circuit, $\beta = 55$, $V_{BE} = 0.7V$



$$I_c \approx I_B = \frac{V_{EE} - V_{BB}}{R_E + R_B/\beta}$$

$$= \frac{20 - 0.7}{10^4 + 10^5/55}$$

$$= \frac{13 \times 10^{-3}}{10 + 100/55}$$

$$= 1.73 \times 10^{-3} A$$

$$= 1.73 mA$$

$$V_C = V_{CC} - I_C R_C$$

$$= 20 - (1.73 \times 10^{-3})(4.7 \times 10^3)$$

$$= 11.92 V$$

$$\rightarrow V_E = -V_{EE} + I_E R_E = -20 + (1.73 \times 10^{-3})(10 \times 10^3) = -2.7 V$$

$$\rightarrow V_{CE} = V_C - V_E = 11.92 - (-2.7)$$

$$= 14.62 V$$

Q point $\rightarrow [14.62, 1.73 \text{ mA}]$