

# Tutorial - 2 (U20CS108)

Page No.:	1
Date:	youva

Dheeraya Ozar


- ① The diffusion constant for holes in Si is  $13 \text{ cm}^2/\text{sec}$ . What is the diffusion current density if the gradient of the hole concentration,  $\frac{dp}{dx} = -2 \times 10^{14} \text{ holes/cm}^3/\text{cm}$ ?

$$J_p = -e \times D_p \times \frac{dp}{dx}$$

$$D_p = 13 \text{ cm}^2/\text{sec}$$

$$\begin{aligned} J_p &= + (1.6 \times 10^{-19}) \times 13 \times (-2 \times 10^{14}) \text{ holes/cm}^3 \\ &= -4.16 \text{ A/cm}^2 \\ &= -0.416 \text{ mA/cm}^2 \end{aligned}$$

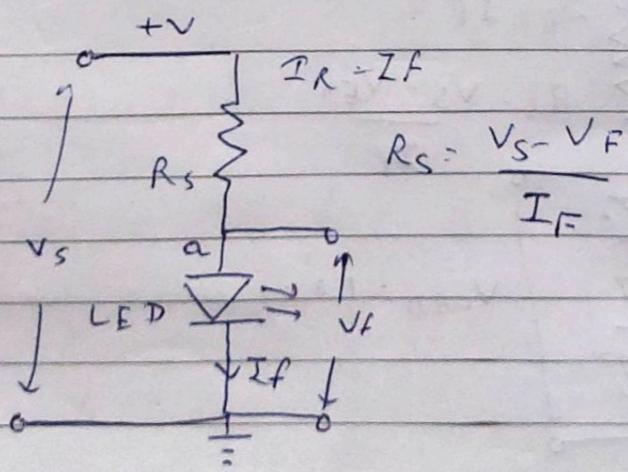- ② An amber coloured LED with forward voltage drop of 2 to 5-0 v dc supply. find series resistor to forward current less than 10 mA. Also flowing through the diode if a 100  $\Omega$  series resistor.



→ Series resistor at 10mA

$$R_s = \frac{V_s - V_f}{I_f}$$

$$\Rightarrow \frac{5 - 2}{10 \times 10^{-3}}$$

$$= \underline{300 \Omega}$$

→  $100 \Omega = R$

$$R_s = \frac{V_s - V_f}{I_f}$$


$$I_f = \frac{V_s - V_f}{R_s}$$

$$= \frac{5 - 2}{100}$$

$$= 30 \times 10^{-3} A$$

$$= 30 mA$$

(3)

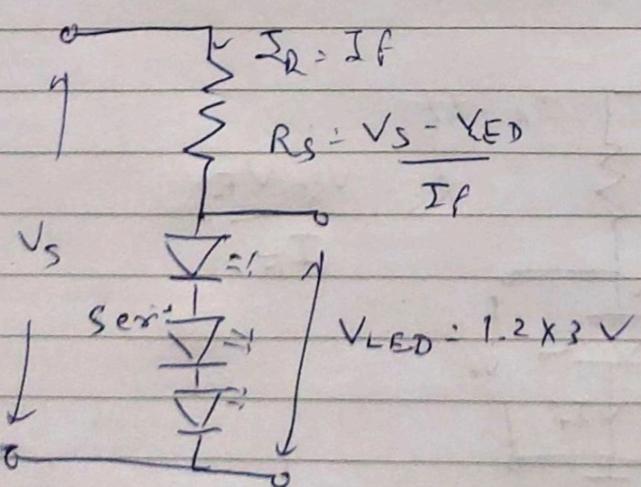

—  $V_{LED} = 3 \times 1.2 = 3.6 \text{ V}$


$R_S = V_S - V_{LED} = 1.4 \text{ volts}$

$V_{LED}$  using upper formula

$$R_S = \frac{V_S - V_{LED}}{I_F}$$

- Here, we assumed LEDs have 5V device with forward current of about 10mA.

(4)

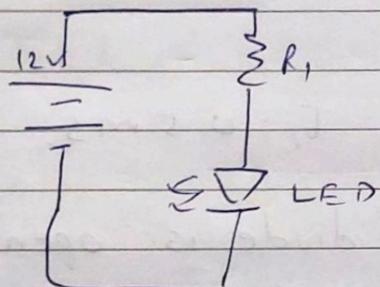

LED forward Voltage: 3.9V

LED forward current: 1400mA

→ The resistor has voltage drop =  $12 - 3.9 = 8.1 \text{ V}$


(LED)


Now, Power Rating =  $i \times v$

$$= 8.1 \times 1400 \times 10^{-3}$$

$$= \underline{\underline{11.34 \text{ Watts}}}$$

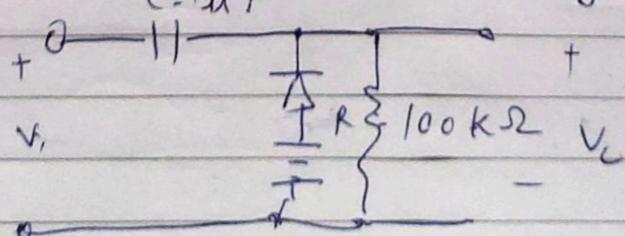(5) Determine  $V_o$  for following circuit (ideal diode)



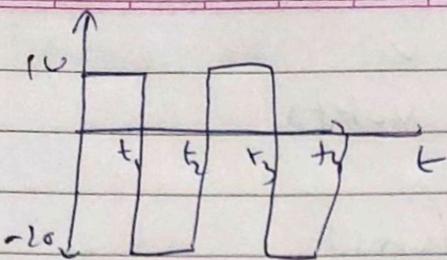

→ frequency = 1000 Hz

$$T = \frac{1}{f}$$


$$= \frac{1}{1000}$$

$$= 1 \text{ ms}$$

so, for each interval  $t_i = 0.5 \text{ ms}$ .


- ① for first interval, diode is open circuit,  
no current at output,  $V_o = 0$

→  $0 < t < t_1, V_i > 10V, V_D = 0$

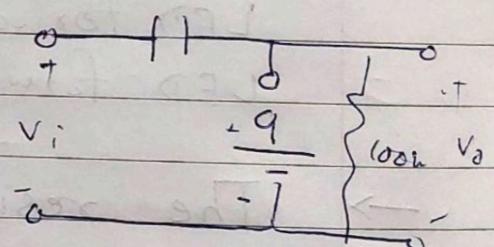


- ② for 2<sup>nd</sup> interval, diode is short circuit,  
 $V_R = V_o = 5V$
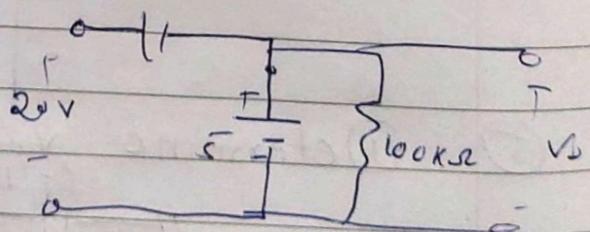
$$\begin{aligned} V &= -V_o + V_C = -5 = 0 \\ \therefore V_C &= 25V \end{aligned}$$



③ for 3<sup>rd</sup> interval, diode open circuit.

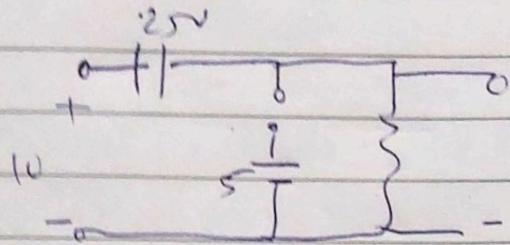$I_R$  will produce, so  $10 + 25 - V_o = 0$   
 $\therefore V_o = 35V$



Discharge time  $t = RC$   
 $= 100 \times 10^3 \times 10^{-3} \times 0.1 = 10ms$

$\therefore$  Total discharge  $5t = 5 \times 10ms = 50ms >>$  interval time

