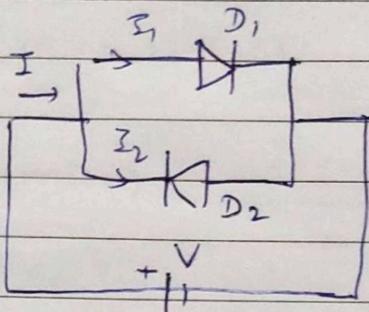


Tutorial - I

Q-1 In the circuit below, Current voltage relationship when D_1 and D_2 are identical given by (for diode)



→ diode current equation is:

$$I = I_0 (e^{\frac{V_D}{nV_T}} - 1)$$

$I_2 = I_0$ (Reverse Saturation current).

$$I_1 = I_0 (e^{\frac{V_D}{V_T}} - 1) \quad (n=1 \text{ for Ge diode})$$

$$\text{Now } I = I_1 + I_2$$

$$\therefore I = I_0 (e^{\frac{V}{V_T}} - 1) + I_0$$

$$\therefore I_0 = I_0 e^{\frac{V}{V_T}} - I_0 + I_0$$

$$\therefore \frac{I}{I_0} = e^{\frac{V}{V_T}}$$


$$\therefore \ln\left(\frac{I}{I_0}\right) = \ln\left(e^{\frac{V}{V_T}}\right)$$

$$\therefore \ln\left(\frac{I}{I_0}\right) = \frac{V}{V_T}$$


$$\therefore V = V_T \ln\left(\frac{I}{I_0}\right) \approx \frac{kT}{q} \ln\left(\frac{I}{I_0}\right)$$

Q-② A PN junction with a $100\ \Omega$ resistor, forward biased so that 100 mA flows. If voltage across this combination is instantaneously reversed to 10 V at $t=0$, the reverse current flows through the diode $t=0$ is approx given by.


for $t > 0$

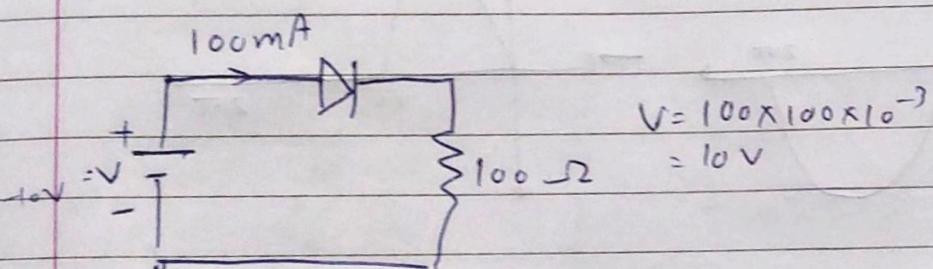

for $t = 0$

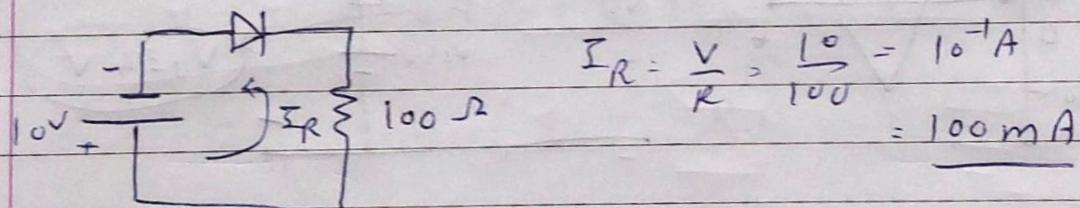


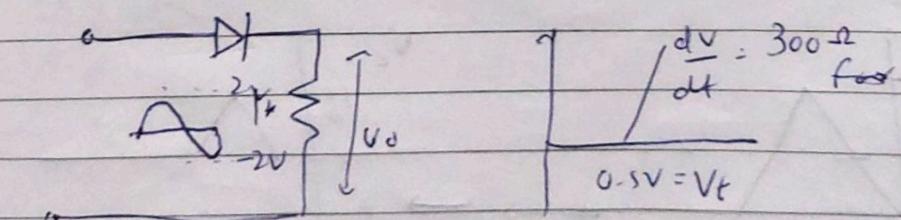Q-③ Consider the circuit shown in figure. if the diode used here has the $V-I$ characteristic V_t graph



$$V_t = 300\ \Omega$$

$$V_t = 0.5\text{ V}$$

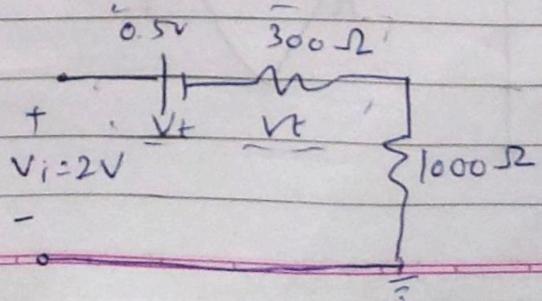

$S_0, V_o = 1.15 \text{ Volt}$


here $i = \frac{V_i - 0.5}{1300}$

$$i = \frac{1.5 - 0.5}{1300} = 1.15 \text{ mA}$$


$$V = 1.1 \text{ mA} (1000)$$

$$= 1.15$$


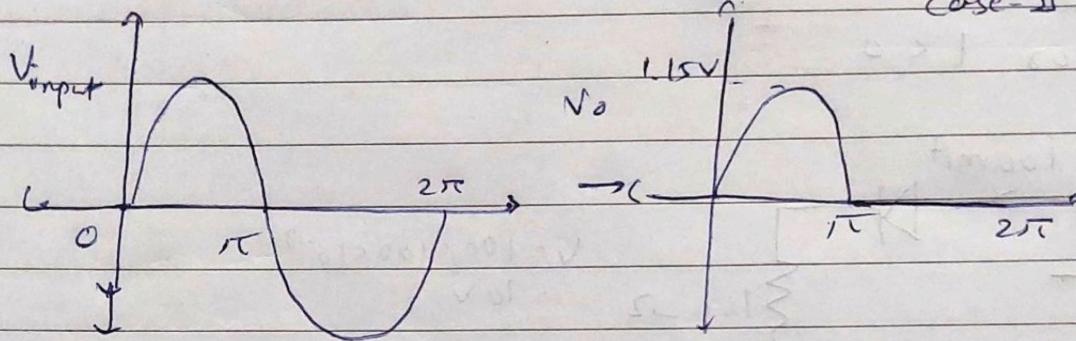
and $V_o = 0$ for $\pi \rightarrow 2\pi$
Case-II




Q. ④

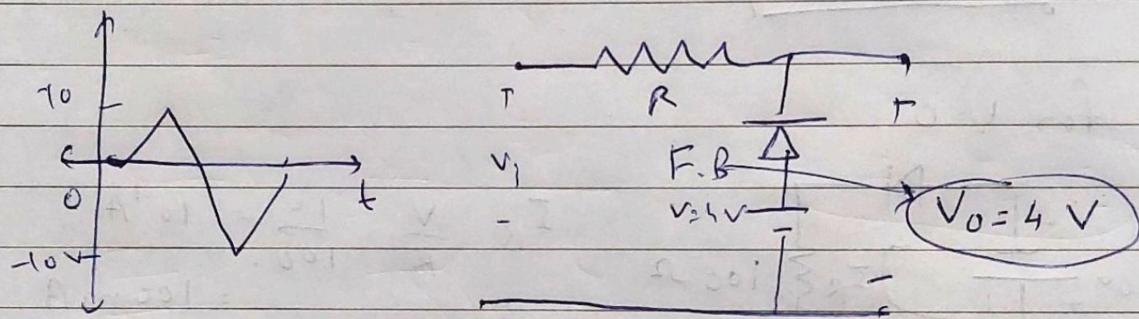


for R.B

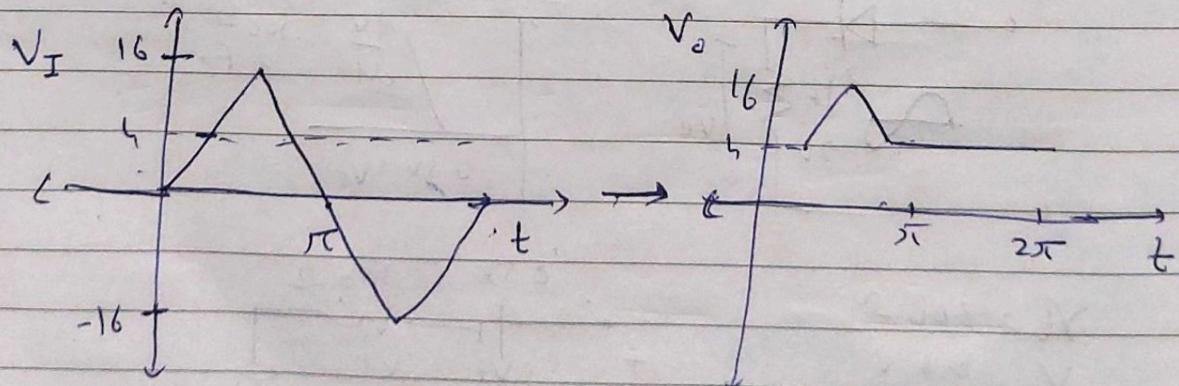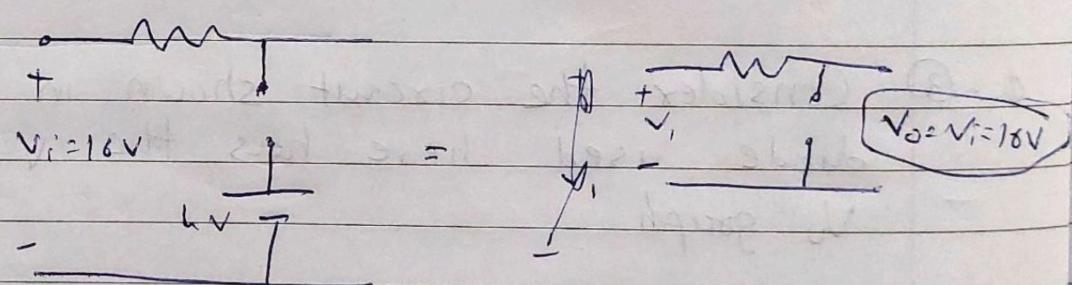

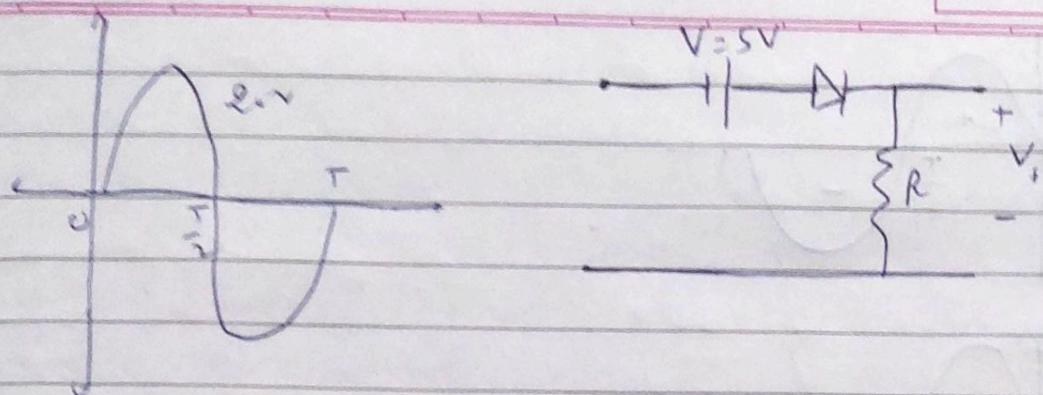


- Case 1 - from 0 to $\frac{T}{2}$ F.B


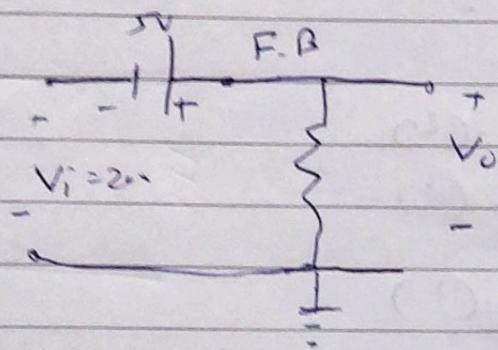


$$V_o = V_i + V = 20 + 5 = 25V$$

- Case 2 - from $\frac{T}{2}$ to T R.B

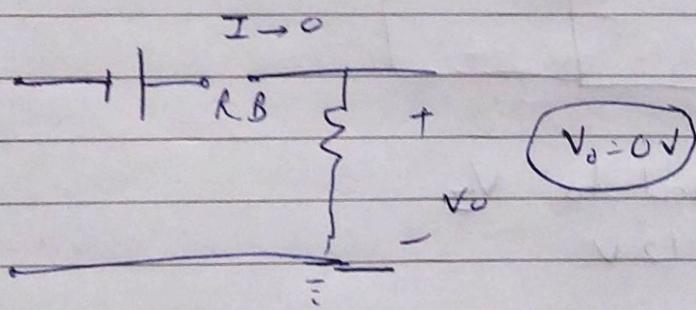

25t

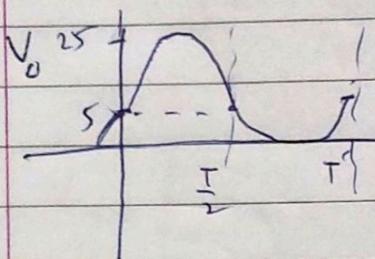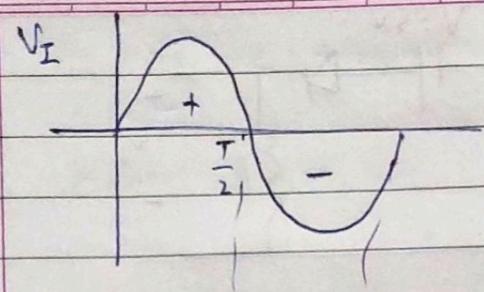


Q-5

$$R_S = 240 \Omega \quad V_L = C^2$$

$$V_S = 30 V \quad V_{RS} = (?)$$

$$V_Z = 12 V \quad I_Z = C^2$$

$$R_L = 580 \Omega \quad$$

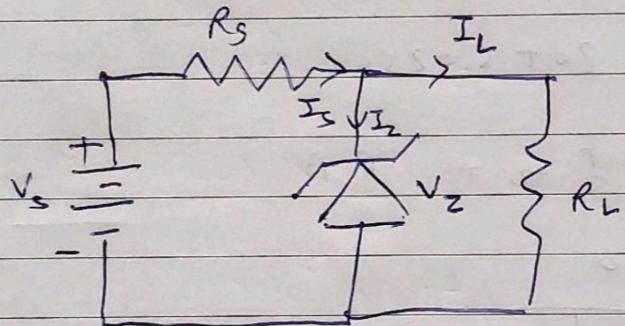

$$\rightarrow I_S = I_L + I_Z$$

$\rightarrow V_L$ is equal to V_Z

$$\therefore V_L = V_Z = 12 V$$

\rightarrow Now V_{RS} is basically,

$$I_S = I_L + I_Z \quad I_S = \frac{V_S - V_Z}{R_S}$$

$$= \frac{30 - 12}{240} = \underline{0.075 A}$$

$$\begin{aligned} V_{RS} &= I_S \cdot R_S \\ &= 0.075 \times 240 \\ &= \underline{0.18V} \end{aligned}$$


$$I_S = 0.075A = 75mA$$

$$I_L = \frac{12}{500} = 24mA$$

$$\begin{aligned} I_Z &= I_S - I_L \\ &= 75 - 24 \\ &= 51mA \end{aligned}$$

$$V_L = 12, V_{RS} = 18V, I_Z = 51mA$$

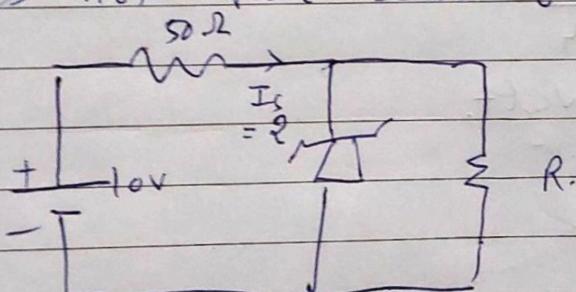Q-⑥ The 6 volts zener diode shown in figure has zero zener resistance and knee current of 5 mA. R_{min} so that Voltage across it does not fall below 6 volts.



$$V_Z = 6V \quad I_S = \frac{10 - 6}{50}$$

$$\begin{aligned} I_Z &= 5mA \\ &\quad - \frac{5}{50} \\ &= 80mA \end{aligned}$$

$$I_R = 80 - 5 = 75mA$$

$$R_{min} = \frac{V}{I_R} = \frac{6}{75 \times 10^{-3}} = \underline{\underline{80\Omega}} \quad \text{So } R_{min} = 80$$

Q-7 Find the range of load current and resistance that will maintain $V_o = 10\text{ V}$, Power Max across zener diode

$$\text{given} \rightarrow V_i = 50\text{ V}$$

$$V_o = 10\text{ V}$$

$$\therefore I = \frac{50 - 10}{1 \times 10^{-3}} = 40\text{ mA}$$

$$I_L = 4(-I_z)\text{ mA}$$

$$P = I^2 R = (40 - I_z)^2 R$$

$$R \rightarrow V = I \times R$$

$$10 = 40 \times R$$

$$R = 0.25\text{ k}\Omega$$

$$\begin{aligned} P &= (10)^2 \times \frac{10^3}{4} \\ &= 4 \times 10^5 \text{ Watt.} \end{aligned}$$

