

## DELD Tutorial-3

Q-①

In a common base connection,  $I_E = 1 \text{ mA}$ ,  $I_C = 0.95 \text{ mA}$ ,  $I_B = (?)$

→ In common base connection,  $I_E = I_B + I_C$

$$\begin{aligned} I_B &= I_E - I_C \\ &= 1 \text{ mA} - 0.95 \text{ mA} \\ &= 0.05 \text{ mA} \end{aligned}$$

Q-②

In a common base connection,  $\alpha = 0.9$ ,  $I_E = 1 \text{ mA}$ , determine  $I_B$ :

→ In a common base connection  $\alpha = 0.9$ ,  $I_E = 1 \text{ mA}$

$$\text{Now } \alpha = \frac{I_C}{I_E}$$

$$\begin{aligned} I_C &= \alpha I_E \\ &= 0.9 \times 1 = 0.9 \text{ mA} \end{aligned}$$

$$\text{Now, } I_E = I_B + I_C$$

$$\begin{aligned} I_B &= I_E - I_C \\ &= 1 - 0.9 \\ &= 0.1 \text{ mA} \end{aligned}$$

Q-③ In a common base connection,  $I_C = 0.95 \text{ mA}$ ,  $I_E = 0.05 \text{ mA}$ ,  $\alpha = (?)$

$$\rightarrow I_E = I_B + I_C = 0.05 + 0.95 = 1 \text{ mA}$$

$$\therefore \alpha = \frac{I_C}{I_E} = \frac{0.95}{1} = 0.95$$

Q. (4) In a CB connection,  $I_E = 1 \text{ mA}$ ,  $I_{CBO} = 50 \mu\text{A}$ ,  $\alpha = 0.92$ , Find total collector current.

→ Here  $I_E = 1 \text{ mA}$ ,  $\alpha = 0.92$ ,  $I_{CBO} = 50 \mu\text{A}$

$$\begin{aligned} \rightarrow \text{Total collector current } I_C &= \alpha I_E + I_{CBO} \\ &= (0.92 \times 1 + 50 \times 10^{-3}) \text{ mA} \\ &= \underline{\underline{0.97 \text{ mA}}} \end{aligned}$$

Q. (5) Find  $\beta$  if (i)  $\alpha = 0.9$  (ii)  $\alpha = 0.98$  (iii)  $\alpha = 0.99$


$$\beta = \frac{\alpha}{(1-\alpha)}$$

$$(i) \alpha = 0.9 \rightarrow \beta = \frac{0.9}{1 - 0.9} = \frac{0.9}{0.1} = \underline{\underline{9}}$$

$$(ii) \alpha = 0.98 \rightarrow \beta = \frac{0.98}{1 - 0.98} = \frac{0.98}{0.02} = \underline{\underline{49}}$$

$$(iii) \alpha = 0.99 \rightarrow \beta = \frac{0.99}{1 - 0.99} = \frac{0.99}{0.01} = \underline{\underline{99}}$$

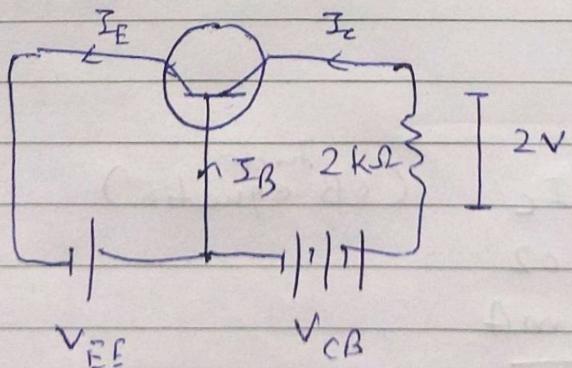Q. (6) In a CB junction,  $\alpha = 0.95$ , Voltage drop across  $2\text{k}\Omega$  resistance which is connected in the collector is 2V. Find  $I_B$ .



$$\rightarrow V_{RC} = 2V \text{ (across } 2k\Omega)$$

$$\therefore I_C = \frac{2}{2k\Omega} = 1mA$$

$$- \alpha = \frac{I_C}{I_E}$$

$$\begin{aligned} \therefore I_E &= \frac{\alpha I_C}{\alpha} \\ &= \frac{1}{0.95} \approx 1.05mA \end{aligned}$$

$$- \text{ Now } I_B = I_B + I_C$$

$$\begin{aligned} \therefore I_B &= I_E - I_C = 1.05 - 1 \\ &= \underline{0.05mA} \end{aligned}$$


Q-⑦ Calculate  $I_E$ ,  $\beta = 50$ ,  $I_B = 20\mu A$ .

$$- \beta = \frac{I_C}{I_B}$$

$$\begin{aligned} I_C &= \beta I_B \\ &= 50 \times 0.02 \\ &= 1mA \end{aligned}$$

$$\begin{aligned} \text{Hs } I_E &= I_B + I_C \quad (\text{B}^{\text{Junction}} \text{ equation}) \\ &= 1 + 0.02 \\ &= \underline{1.02mA} \end{aligned}$$

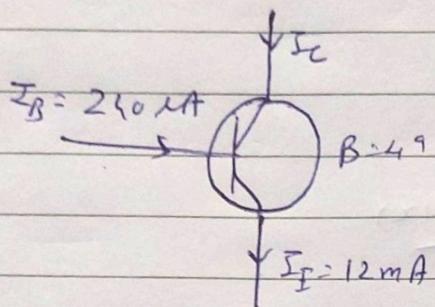Q-8 Find the  $\alpha$  rating of the transistor shown in fig. Hence find  $I_C$  both  $\text{using}$   $\alpha$ ,  $\beta$ .



$$\beta = \frac{\alpha}{1-\alpha}$$

$$\therefore (1-\alpha)\beta = \alpha$$

$$\beta - \alpha\beta = \alpha$$

$$\therefore \beta = \alpha(1+\beta)$$

$$\therefore \alpha = \frac{\beta}{1+\beta}$$

$$\begin{aligned} \alpha &= \frac{49}{1+49} \\ &= \underline{0.98} \end{aligned}$$

$$\text{Now, } \alpha = \frac{I_C}{I_E}, \quad \beta = \frac{I_C}{I_B}$$

$$\therefore I_C = \alpha I_E = 0.98(12) = 11.76 \text{ mA}$$

$$\therefore I_C = \beta I_B = 240(\mu\text{A})(49) = \underline{11.76 \text{ mA}}$$

Q. ⑨ A transistor has the following ratings

$$I_c(\text{max}) = 500 \text{ mA}$$

$$\beta(\text{max}) = 300$$


$$I_B(\text{max}) = (?)$$

$$\rightarrow I_B(\text{max}) = \frac{I_c(\text{max})}{\beta}$$

$$I_B(\text{max}) = \frac{500}{300} \text{ mA}$$


$$= 1.67 \text{ mA}$$

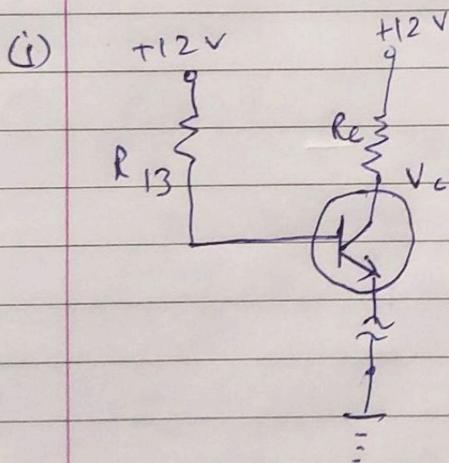Q. ⑩ Fig shows open circuit failures. Explain behaviors.




— This circuit is basically open emitter failure here collector diode is not forward biased, it is off and there can be neither collector current nor base current. Therefore No voltage drop across  $R_C$  and  $V_{BE}$  and  $V_C$  will be 12V

(ii)

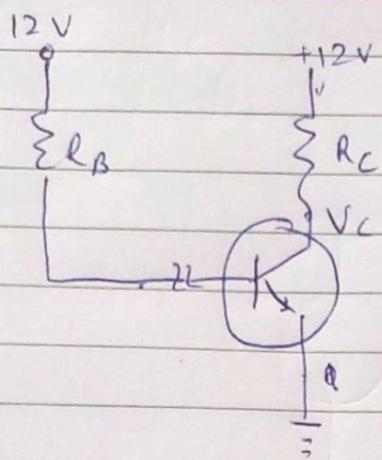

- This figure is basically open base failure in a transistor. Here  $I_B = 0$  because Base is open and therefore transistor is in cut-off and all currents are 0A,  $V_B = 0$  and  $V_C = 12V$  here.

(iii)

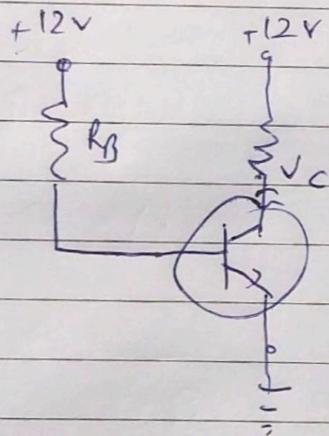

- This figure shows open collector failure in a transistor. Here emitter diode is still on, so we expect to see 0.7V at the base, we will see  $V_B = 12V$  because  $I_B = 0$ .